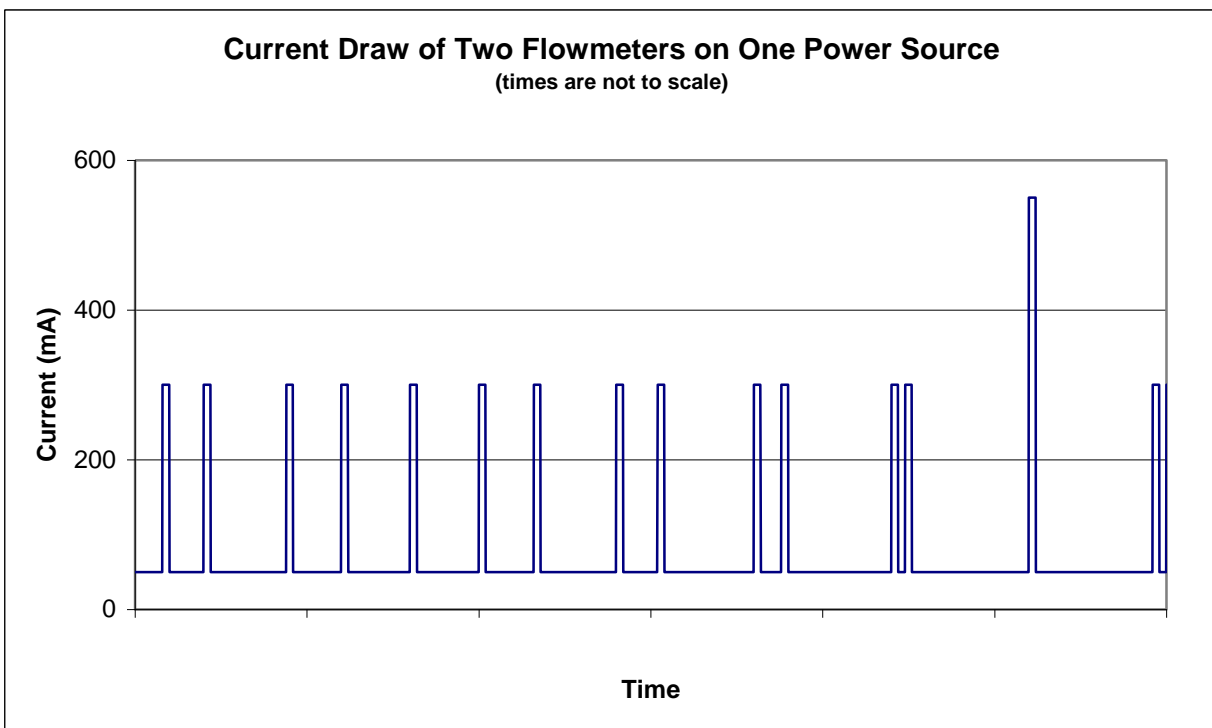



Attaching Multiple 4200 Series Meters to one Power Source

Application Note—August 2004

The flowmeter draws a 20 microsecond pulse of current of 250 mA on top of 50 mA steady state current. The power supply needs to be capable of supplying at least 10.0V during current pulses (11.4V for the intrinsically safe versions). If multiple meters attached to the same power source, then these pulses occasionally will become in phase. Typically a switching power supply without a linear regulator on the output will not be fast enough to adjust to this sudden change in current. Also, most capacitors have too much series resistance to overcome this and could degrade because of the frequent charging and discharging. Using a slightly higher output on the switching power supply output and a simple 12V linear regulator (like a National Instruments LM340A) should work in most cases.



Example Circuit

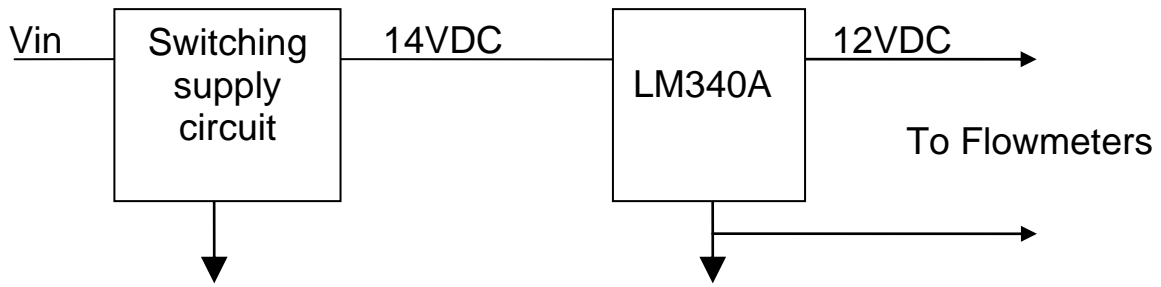

TSI Incorporated – 500 Cardigan Road, Shoreview, MN 55126 U.S.A

USA	Tel: +1 800 874 2811	E-mail: info@tsi.com	Website: www.tsi.com
UK	Tel: +44 149 4 459200	E-mail: tsiuk@tsi.com	Website: www.tsiinc.co.uk
France	Tel: +33 491 11 87 64	E-mail: tsifrance@tsi.com	Website: www.tsiinc.fr
Germany	Tel: +49 241 523030	E-mail: tsigmbh@tsi.com	Website: www.tsiinc.de
India	Tel: +91 80 41132470	E-mail: tsi-india@tsi.com	
China	Tel: +86 10 8260 1595	E-mail: tsibeijing@tsi.com	
Singapore	Tel: +65 6595 6388	E-mail: tsi-singapore@tsi.com	



TRUST. SCIENCE. INNOVATION.

Contact your local TSI Distributor or visit our website www.tsi.com for more detailed specifications.